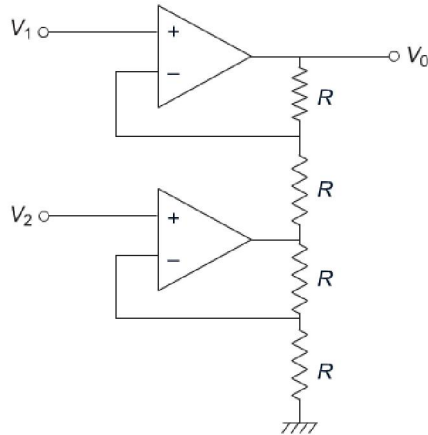



Solved Problems on Op-Amp

Q1:

Show that $V_0 = 2(V_1 - V_2)$.



The circuit can be drawn as given below.

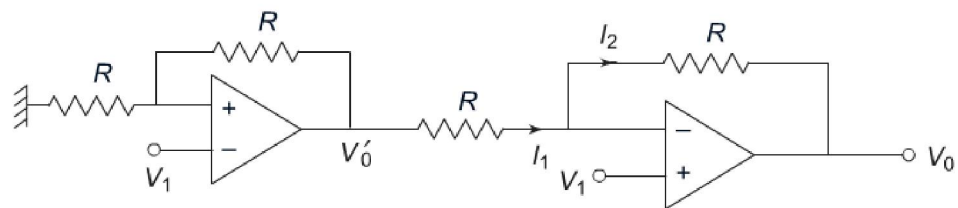

$$\frac{V'_0}{V_2} = \text{Gain} = \frac{R_1 + R_2}{R_1} = \frac{2R}{R} = 2$$

$$V'_0 = 2V_2$$

$$\frac{V'_0 - V_1}{R} = \frac{V_1 - V_0}{R} = 2V_1 = -V'_0 - V_0$$

$$\Rightarrow 2V_1 = (V'_0 + V_0)$$

$$2V_1 = 2V_2 + V_0$$

$$\Rightarrow V_0 = 2(V_1 - V_2)$$

==

Q2:

For an op-amp integrator with $R = 100 \text{ M}\Omega$ and $C = 1 \text{ }\mu\text{F}$, an input of $2 \sin 1000 t$ is applied. Determine the value of v_o .

Given

$$v_i = 2 \sin 1000 t$$

$$R = 100 \text{ M}\Omega$$

$$C = 1 \text{ }\mu\text{F}$$


Required; V_o .

$$v_o = 20 \text{ }\mu\text{V}$$

$$I_1 + I_2 = 0$$

$$I_1 = -I_2$$

$$I_2 = \frac{V_o - V_a}{Z_f}$$

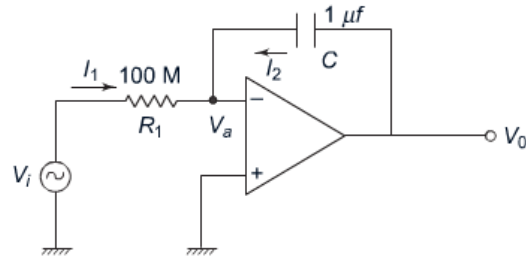

$$I_2 = \frac{cdV_0}{dt}$$

$$I_1 = -I_2$$

$$\frac{v_i}{R} = -\frac{cdV_0}{dt}$$

$$I_1 = \frac{v_i - v_a}{R}, V_o = 0$$

$$I_1 = \frac{v_i}{R}$$

V_i = Input voltage

V_o = Output voltage

V_a = Voltage at the inverting terminal

= 0 V \because Non-inverting terminal is grounded.

$$\frac{v_i}{R} = -c \frac{dV_0}{dt}$$

$$\Rightarrow -\frac{v_i}{RC} = \frac{dv_0}{dt} = \int \frac{dV_0}{dt} - \int \frac{V_i}{RC} dt$$

$$\Rightarrow v_0 = -\frac{1}{RC} \int_0^1 V_i dt$$

$$v_0 = -\frac{1}{RC} \int_0^1 V_i dt$$

$$= \frac{-1}{(100 \times 10^6)(10^{-6})} \int_0^1 2 \sin 1000 t dt$$

$$= \frac{-1}{100} \int 2 \sin 1000 t dt$$


$$= \frac{-1}{50} \int \sin 1000 t dt$$

$$= \frac{-1}{(50)(1000)} \cos 1000 t$$

$$|v_0| = \frac{1}{50000} = 20 \text{ }\mu\text{V}$$

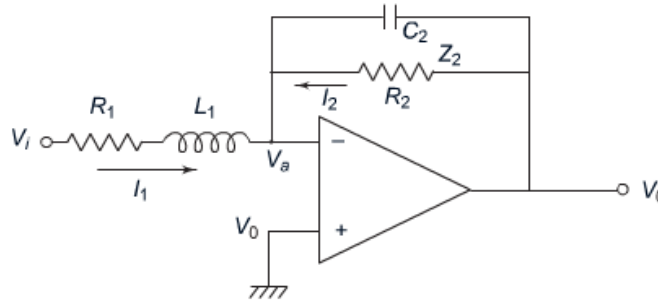Q3: (assignment Q 2)

An op-amp has R_1 and L_1 in series on the input side, connected to the inverting terminal and R_2 , C_2 connected in parallel in the feedback path. The non-inverting terminal is grounded. Derive the transfer function.



Hint:

$$I_1 + I_2 = 0 \Rightarrow I_1 = -I_2$$

$$Z_1 = R_1 + j\omega L_1$$

$$I_1 = \frac{v_i}{Z_1} = \frac{v_i}{R_1 + j\omega L_1}$$

$$Z_2 = \frac{R_2 \cdot \frac{1}{j\omega c_2}}{R_2 + \frac{1}{j\omega c_2}}$$

$$Z_2 = \frac{R_2 / j\omega c_2}{j\omega c_2 R_2 + 1}$$

$$I_2 = \frac{v_0}{Z_2} = \frac{v_0}{\frac{R_2}{j\omega R_2 c_2 + 1}}$$

$$I_2 = v_0 \frac{(j\omega R_2 c_2 + 1)}{R_2}$$

$$I_1 = -I_2$$

And $A_v = V_o/V_i$

Q4: (Assignment Q 3)

Q3: In figure 3, find out the expression for current in R2.

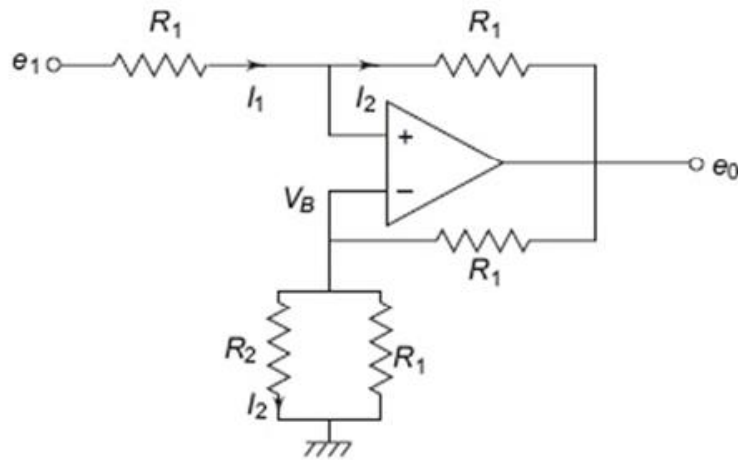


Figure 3.


Hint:

$$V_B = \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{e_0}{R_1} + \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \frac{\frac{e_0 R_1 R_2}{R_1 + R_2}}{R_1 \left(1 + \frac{R_2}{R_1 + R_2} \right)}$$

$$V_B = e_0 \frac{R_2}{R_1 + 2R_2}$$

Then apply KCL to get e_1 and V_B . Then current through R2 can be calculated.

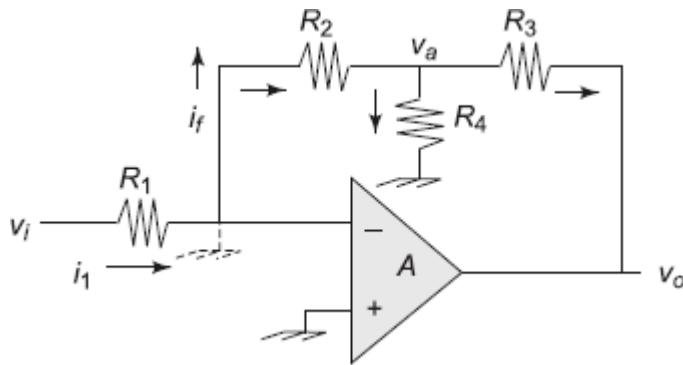Q 5: find the value of Closed loop gain in the amplifier shown below



Ans:

$$\frac{v_i}{R_1} = -\frac{v_a}{R_2}$$

$$v_a = -\frac{R_2}{R_1} v_i$$

$$\left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) v_a = \frac{v_o}{R_3} + \frac{0}{R_2}$$

$$v_o = \left(1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right) v_a$$

$$= -\left(1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right) \frac{R_2}{R_1} v_i$$

$$\frac{v_o}{v_i} = -\frac{R_F}{R_1} = -\frac{R_2 + R_3 + \frac{R_2 R_3}{R_4}}{R_1}$$

If $R_1 = R_2 = R_3 = 1 \text{ K}$, $R_4 = 10 \text{ } \Omega$,

then $R_F = 2 \text{ K} + 1 \text{ M}/10 = 2 \text{ K} + 100 \text{ K}$

$= 102 \text{ K}$, voltage-gain

$$= A_v = \frac{v_o}{v_i} = -\frac{102 \text{ K}}{1 \text{ K}} = -102$$