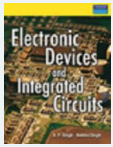


## This Book

Electronic Devices  
and Integrated  
Circuits

## Search

## Contents

• Table of Contents
• Index
Copyright
Dedication
Preface
Acknowledgements
► Ch. 1. Physics of Semiconductors
► Ch. 2. Physical Phenomenon in Homojunction
► Ch. 3. Diode as Circuit Element
► Ch. 4. Junction Diode Rectifier
► Ch. 5. Physical Phenomenon in BJT
► Ch. 6. Physical Phenomenon in JFET and MOSFET
► Ch. 7. Biasing
► Ch. 8. BJT Amplifiers
► Ch. 9. FET Amplifiers
► Ch. 10. Frequency Response of BJT Amplifiers
► Ch. 11. Multistage Amplifiers
► Ch. 12. Feedback in Amplifiers
► Ch. 13. Oscillators
► Ch. 14. Power Amplifiers
▼ Ch. 15. Operational Amplifier
15.1. Introduction
15.2. Ideal Characteristics of Operational Amplifier
15.3. Frequency Response of Op-amp
15.4. Offset Voltage
15.5. Inverting Op-amp Circuit
15.6. Summing Op-amp Circuit
15.7. Op-amp Integrator & Differentiator
15.8. Non-linear Applications of Op-amps
15.9. Precision Rectifier
15.10. Square Waveform Generation
15.11. Analog Multiplier
15.12. Filters
15.13. Simulated Inductance Approach
15.14. DVCVS/DVCCS
15.15. BiFET and BiMOS Circuits
15.16. Analog Computer
<b>15.17. SOLVED PROBLEMS</b>
► Ch. 16. Regulated Power Supplies
► Ch. 17. Integrated Circuit Timers



## Chapter 15. Operational Amplifier &gt; SOLVED PROBLEMS

SHARE

URL

SHOW SEARCH TERMS

## 15.17. SOLVED PROBLEMS


1. The output of an op-amp integrator can swing from +15 V to -15 V. The step input shown in **Fig. 15.100(a)** is  $v_i = 0$  for  $t < 0$  and switched at  $t = 0$  to 5 V. The output voltage  $v_o = +15$  V for  $t < 0$ . Plot the waveform.

*Solution:*

$$v_o = -\frac{1}{RC} \int v_i dt + C = -\frac{v_i}{RC} t + C$$

$$\text{At } t \leq 0, v_i = 0 \text{ and } v_o = +15 \text{ V, } v_o = 15$$

$$= -\frac{v_i}{RC} * 0 + C$$

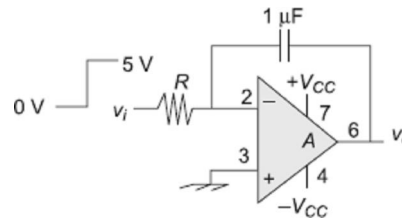**Figure 15.100(a).** **Figure 15.100(a)**

$$0 = -\frac{v_i}{RC} t + 15 \text{ and}$$

$$t = \frac{15}{v_i} RC = \frac{15}{5} 1 \text{ K} \times 10^{-6} = 3 \text{ ms}$$

The time at which the  $v_o = -15$ 

$$= -\left(\frac{v_i}{RC}\right) t + 15$$


$$t = \frac{30}{v_i} RC = \frac{30}{5} 1 \text{ K} \times 10^{-6} = 6 \text{ ms}$$

*Solution:*Writing node equations at node  $v(-)$  of  $A_1$ 

$$v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{v_2}{R_3} + \frac{v_3}{R_1}$$

$$C = 15 \text{ V, } v_o = -\frac{v_i}{RC} t + 15,$$

► Ch. 18. Special Two-terminal Devices
► Ch. 19. Tuned Amplifier
► Bibliography
Index

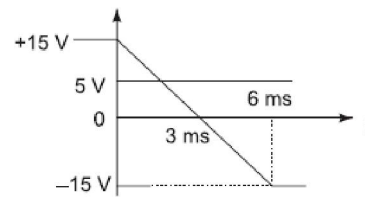
**Figure 15.100(b). Figure 15.100(b)**

Now the waveform is plotted as in **Fig. 15.100(b)**.

2. For the instrumentation amplifier shown in **Fig. 15.101**, using two ideal op-amps verify the following equation

(GKP Univ. 1994).

$$v_o = \left( 1 + \frac{R_2}{R_1} + \frac{2R_2}{R_3} \right) (v_2 - v_1)$$

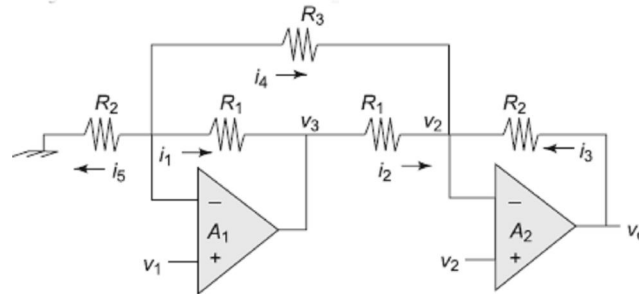**Figure 15.101. Two op-amp instrumentation amplifier**

At node  $v_{(-)}$  of  $A_2$

At node  $v_{(-)}$  of  $A_2$

$$v_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{v_o}{R_2} + \frac{v_3}{R_1} + \frac{v_1}{R_3}$$

Subtracting this equation from previous one yields

$$\begin{aligned} & \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) (v_1 - v_2) + \frac{1}{R_3} (v_1 - v_2) \\ &= -\frac{v_o}{R_2} \\ & \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{2}{R_3} \right) (v_1 - v_2) = \frac{-v_o}{R_2} \end{aligned}$$

**Solution:**

From **Fig. 15.102**

$$v_{o2}^* = \frac{KR_2 v_{o2}}{KR_2 + R_2} = \frac{Kv_{o2}}{K+1}$$

$$v_{o1} = v_1 + aR_1 i, \quad v_{o2} = v_2 - bR_1 i,$$

$$\text{where, } i = \frac{v_1 - v_2}{R}$$

$$v_{o1} = v_1 + a \frac{R_1}{R} (v_1 - v_2)$$


$$= \left(1 + a \frac{R_1}{R}\right) v_1 - a \frac{R_1}{R} v_2$$

$$v_{o2} = v_2 - b \frac{R_1}{R} (v_1 - v_2)$$

$$v_o = \left(1 + \frac{R_2}{R_1} + \frac{2R_2}{R_3}\right) (v_2 - v_1)$$

3. Show that the cross coupled differential voltage follower instrumentation amplifier shown in **Fig. 15.102** produces output voltage  $v_o = (1 + a + b)(v_2 - v_1)$ .

**Figure 15.102. Three op-amp instrumentation amplifier**

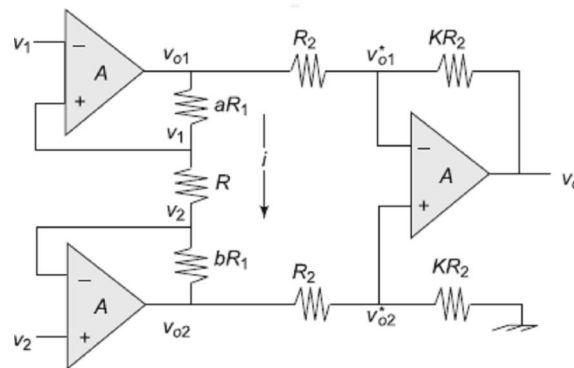

$$= \left(1 + b \frac{R_1}{R}\right) v_2 - b \frac{R_1}{R} v_1$$

$$v_o = \frac{-KR_2}{R_2} v_{o1} + \left(1 + \frac{KR_2}{R_2}\right) \left(\frac{Kv_{o2}}{1+K}\right)$$

$$= -Kv_{o1} + Kv_{o2} = K(v_{o2} - v_{o1})$$

$$= K \left\{ \begin{aligned} &\left(1 + b \frac{R_1}{R}\right) v_2 - b \left(\frac{R_1}{R}\right) v_1 \\ &- \left(1 + a \frac{R_1}{R}\right) v_1 + a \left(\frac{R_1}{R}\right) v_2 \end{aligned} \right\}$$

$$= K \left\{ \begin{aligned} &\left(1 + (a+b) \frac{R_1}{R}\right) v_2 \\ &- \left(1 + (a+b) \frac{R_1}{R}\right) v_1 \end{aligned} \right\}$$

$$v_o = (1 + a + b)(v_2 - v_1) \text{ for}$$

$$R = R_1$$

4. Obtain the voltage  $v_o$  for the circuit of **Fig. 15.103**. (AMI 1992).

*Solution:*

Writing node equations as

$$\frac{v_i}{R_1} = -\frac{v_a}{R_2}$$

$$v_a = -\frac{R_2}{R_1} v_i$$

$$\left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) v_a = \frac{v_o}{R_3} + \frac{0}{R_2}$$

$$v_o = \left( 1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right) v_a$$

$$= -\left( 1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right) \frac{R_2}{R_1} v_i$$

$$\frac{v_o}{v_i} = -\frac{R_F}{R_1} = -\frac{R_2 + R_3 + \frac{R_2 R_3}{R_4}}{R_1}$$


If  $R_1 = R_2 = R_3 = 1 \text{ K}$ ,  $R_4 = 10 \Omega$ ,

then  $R_F = 2 \text{ K} + 1 \text{ M}/10 = 2 \text{ K} + 100 \text{ K}$

$= 102 \text{ K}$ , voltage-gain

$$= A_v = \frac{v_o}{v_i} = -\frac{102 \text{ K}}{1 \text{ K}} = -102$$

**Figure 15.103. Figure 15.103**

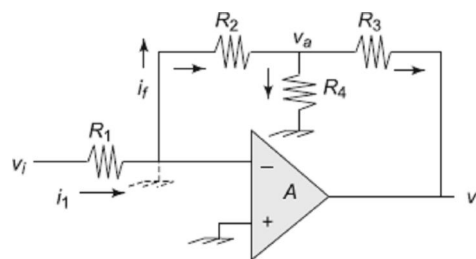

This illustrates that using only few kilo ohm resistances in the form of *T*-network provides very large feedback resistance resulting into very large gain.

5. Obtain the voltage gain  $v_o/v_i$  for **Fig. 15.104(a)**.

*Solution:*

$$\left( \frac{1}{R} + \frac{1}{R_i + R_1} + \frac{1}{R_F} \right) v_1$$


$$= \frac{v_o}{R_F} + \frac{v_i}{R}$$

$$v_2 = \frac{R_1}{R_1 + R_i} v_1$$

$$\text{or } v_2 - v_1 = \frac{R_1}{R_1 + R_i} v_1 - v_1 = -\frac{R_i}{R_1 + R_i} v_1$$

$$\frac{v_o}{A} = v_2 - v_1 = -\frac{R_i}{R_1 + R_i} v_1$$

**Figure 15.104(a). Figure 15.104(a)**

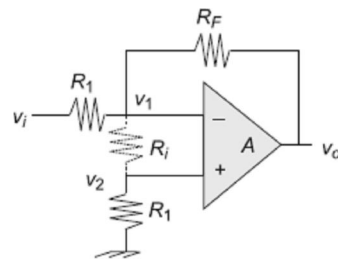

Combining above equations yield

$$\begin{aligned}
 & -\frac{v_o}{A} \times \frac{R_i + R_1}{R_i} \\
 & \times \frac{(R_i + R_1)(R + R_F) + RR_F}{RR_F(R_i + R_1)} - \frac{v_o}{R_F} = \frac{v_i}{R} \\
 & \frac{v_i}{R} = -\frac{(R_i + R_1)(R + R_F) + RR_F + ARR_i v_o}{ARR_F R_i}
 \end{aligned}$$

Hence,


$$\frac{v_o}{v_i} = -\frac{ARR_F R_i}{(R_i + R_1)(R + R_F) + RR_F + ARR_i}$$

6. Obtain the voltage gain  $v_o/v_i$  for **Fig. 15.104(b)**.

*Solution:*

$$\begin{aligned}
 & v_1 \left( \frac{1}{R} + \frac{1}{R_1 + R_i} + \frac{1}{R_F} \right) \\
 & = \frac{v_o}{R_F} + \frac{v_i}{R_1 + R_i} \\
 & v_2 = v_i + (v_1 - v_i) \left( \frac{R_1}{R_1 + R_i} \right) \\
 & = v_1 \left( \frac{R_1}{R_1 + R_i} \right) + v_i \left( \frac{R_i}{R_1 + R_i} \right) \\
 & v_2 - v_1 = -\frac{R_i}{R_1 + R_i} v_1 + \frac{R_i}{R_1 + R_i} v_i \\
 & = \frac{R_i}{R_1 + R_i} (v_i - v_1) \\
 & \frac{v_o}{A} = (v_2 - v_1) = (v_i - v_1) \frac{R_i}{R_1 + R_i}, \\
 & \frac{R_i + R_1}{R_i} \left( \frac{v_o}{A} \right) = (v_i - v_1) \\
 & v_1 = -\left( \frac{v_o}{A} \right) \left( \frac{R_i + R_1}{R_i} \right) + v_i \\
 & \left( \frac{v_o}{A} \right) \frac{R_i + R_1}{R_i}
 \end{aligned}$$

**Figure 15.104(b).** **Figure 15.104(b)**

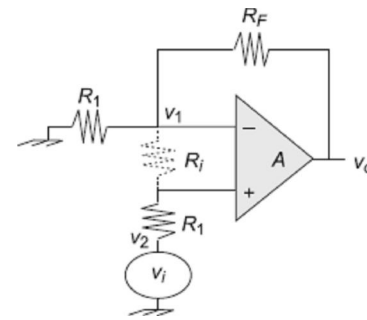


$$\begin{aligned}
 & \times \frac{(R_i + R_1)(R + R_F) + RR_F}{RR_F(R_i + R_1)} \\
 & + \frac{(R_i + R_1)(R + R_F) + RR_F}{RR_F(R_i + R_1)} v_i \\
 & = \frac{v_o}{R_F} + \frac{v_i}{R_i + R_1} \\
 & - \frac{(R_i + R_1)(R + R_F) + RR_F + ARR_i}{ARR_i R_i} v_o \\
 & = - \frac{(R_i + R_1)(R + R_F)}{RR_F(R_i + R_1)} v_i \\
 & \text{Hence, } \frac{v_o}{v_i} \\
 & = - \frac{AR_i(R + R_F)}{(R_i + R_1)(R + R_F) + RR_F + ARR_i}
 \end{aligned}$$

7. Obtain the voltage gain  $v_o/v_{io}$  for **Fig. 15.105**.

*Solution:*

**Figure 15.105. Figure 15.105**

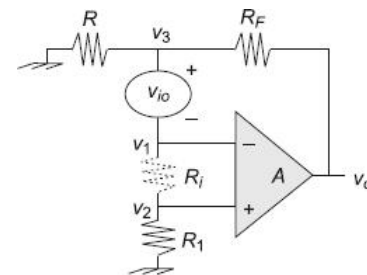

$$\begin{aligned}
 & \frac{v_3 - v_{io}}{R_i + R_1} + \frac{v_3}{R} + \frac{v_3 - v_o}{R_F} = 0 \\
 & v_3 \left( \frac{1}{R_i + R_1} + \frac{1}{R} + \frac{1}{R_F} \right) \\
 & = \frac{v_{io}}{R_i + R_1} + \frac{v_o}{R_F} \\
 & \frac{RR_F + (R_i + R_1)(R + R_F)}{(R_i + R_1)RR_F} v_3
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{v_{io}}{R_i + R_1} + \frac{v_o}{R_F} \\
 v_1 &= v_3 - v_{io} \text{ and } v_2 = \frac{v_3 - v_{io}}{R_i + R_1} R_1 \\
 \frac{v_o}{A} &= v_2 - v_1 = \frac{v_3 - v_{io}}{R_i + R_1} R_1 - v_3 + v_{io} \\
 v_3 &= -\frac{R_i + R_1}{R_i} \times \frac{v_o}{A} + v_{io} \\
 &\left( v_{io} - \frac{v_o}{A} \times \frac{R_i + R_1}{R_i} \right) \\
 &\quad \frac{RR_F + (R + R_F)(R_i + R_1)}{(R_i + R_1)RR_F} \\
 &= \frac{v_o}{R_F} + \frac{v_{io}}{R_i + R_1} \\
 \frac{v_o}{v_{io}} &= \frac{A(R + R_F)R_i}{ARR_i + RR_F + (R + R_F)(R_i + R_1)}
 \end{aligned}$$


8. Prove that the voltage gain and input resistance with feedback in **Fig. 15.106** is given

by the expressions  $A_{vf} = -\frac{AR_F}{R_i(1+A) + R_F}$  and  $R_{if} = \left\{ R_i + \frac{R_F}{1+A} \right\} || R_i$ , where  $R_i$  is the internal input resistance of the op-amp

*Solution:*

$$\begin{aligned}
 i_1 &= \frac{v_i - v_1}{R_1} = i_f = \frac{v_1 - v_o}{R_F} \\
 \frac{v_i}{R_1} + \frac{v_o}{R_F} &= \left( \frac{1}{R_1} + \frac{1}{R_F} \right) v_1 \\
 \text{and } v_o &= -Av_1
 \end{aligned}$$

**Figure 15.106. Figure 15.106**

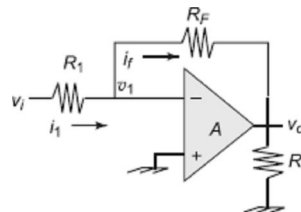

$$\begin{aligned}
\frac{v_i}{R_1} + \frac{v_o}{R_F} &= \left( \frac{1}{R_1} + \frac{1}{R_F} \right) v_1 \\
&= - \left( \frac{1}{R_1} + \frac{1}{R_F} \right) \frac{v_o}{A} \\
\frac{v_i}{R_1} &= - \frac{v_o}{R_F} - \left( \frac{1}{R_1} + \frac{1}{R_F} \right) \frac{v_o}{A} \\
&= - \frac{(1+A)R_1 + R_F}{AR_1R_F} v_o \\
A_{vf} = \frac{v_o}{v_i} &= - \frac{AR_F}{(1+A)R_1 + R_F} \\
v_i - v_1 &= R_1 i_1 \\
v_i + \frac{v_o}{A} &= R_1 i_1 = v_i - \frac{AR_F v_i}{A\{(1+A)R_1 + R_F\}} \\
R_1 i_1 &= \frac{(1+A)R_1 + R_F - R_F}{(1+A)R_1 + R_F} v_i \\
&= \frac{(1+A)R_1}{(1+A)R_1 + R_F} v_i \\
R_{if} = \frac{v_i}{i_1} &= \frac{(1+A)R_1 + R_F}{(1+A)} R_1 \\
&= R_1 + \frac{R_F}{(1+A)}
\end{aligned}$$


This input resistance comes in parallel to the op-amp's internal input resistance  $R_i$ .

Hence, effective input resistance is equal to  $R_{if} = \left\{ R_1 + \frac{R_F}{(1+A)} \right\} \parallel R_i$ .

9. Show that if  $R_i = \infty$ ,  $R_o = 0$  and  $A_1$  and  $A_2 < 0$  in **Fig. 15.107**, then  $v_o = A_2\{A_1(v_f - v_1) + v_2\}$ .

$$\begin{aligned}
\text{where } v_f &= v_o \left( \frac{R_1}{R_1 + R_F} \right). \text{ If } \frac{A_1 A_2 R_1}{R_1 + R_F} \gg 1, \\
\text{then } v_o &= \left( 1 + \frac{R_F}{R_i} \right) \left( v_1 - \frac{v_2}{A_1} \right).
\end{aligned}$$

**Figure 15.107. Figure 15.107**

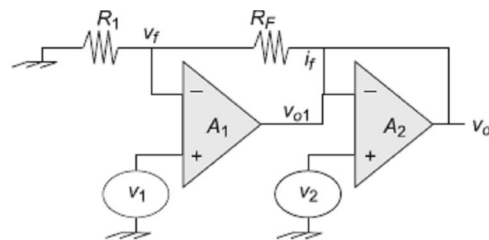

**Solution:**

The output of first op-amp is expressed as  $(v_1 - v_f) A_1 = v_{o1}$

The output of the second op-amp is




$$v_o = A_2(v_2 - v_{o1}) = A_2\{v_2 - A_1(v_1 - v_f)\}$$

$$= A_2\{A_1(v_f - v_1) + v_2\}$$

$$\text{Also, } v_f = \frac{R_1}{R_1 + R_F} v_o$$

$$v_o = A_2 \left\{ A_1 \left( \frac{R_1}{R_1 + R_F} v_o - v_1 \right) + v_2 \right\}$$

**Figure 15.108(a). Figure 15.108(a)**

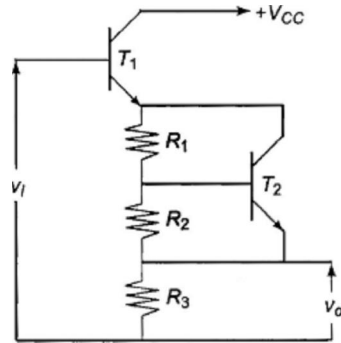

$$v_o - A_2 A_1 \left( \frac{R_1 v_o}{R_1 + R_F} \right) = -A_2(A_1 v_1 - v_2)$$

$$\frac{\{(1 - A_2 A_1) R_1 + R_F\} v_o}{R_1 + R_F} = A_2(v_2 - A_1 v_1)$$

$$v_o = \frac{R_1 + R_F}{R_1} \times \left( v_1 - \frac{v_2}{A_1} \right)$$

$$= \left( 1 + \frac{R_F}{R_1} \right) \left( v_1 - \frac{v_2}{A_1} \right)$$


- 10.** For the dc level shifter circuit shown in **Fig. 15.108(a)**, determine the level shift between input and output voltages.

*Solution:*

$$V_i = V_{BE1} + V_{R_1} + V_{R_2} + V_o,$$

$$V_{BE2} = V_{R_2} = \frac{V_{E_1 E_2}}{R_1 + R_2} R_2$$

**Figure 15.108(b). Figure 15.108(b)**

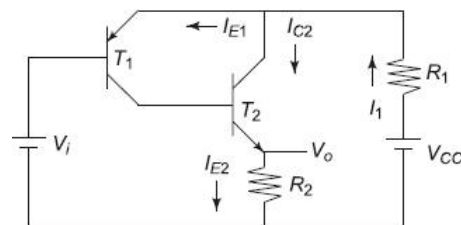

$$\begin{aligned}
 V_o &= V_i - V_{BE1} - V_{E1E2} \\
 &= V_i - V_{BE1} - \left(1 + \frac{R_1}{R_2}\right) V_{BE2} \\
 V_{BE1} &= V_{BE2} = V_{BE} \\
 V_o &= V_i - V_{BE} \left(1 + 1 + \frac{R_1}{R_2}\right) \\
 &= V_i - V_{BE} \left(2 + \frac{R_1}{R_2}\right)
 \end{aligned}$$

11. Obtain the level shift  $V_o$  in **Fig. 15.108(b)**.

*Solution:*


$$\begin{aligned}
 I_1 &= I_{E1} + I_{C2} = I_{C1} + I_{B1} + I_{C2} \\
 &= I_{C1} + I_{B1} + \beta I_{B2} \\
 &= I_{C1} + I_{B1} + \beta I_{C1} \\
 &= I_{B1} + (1 + \beta) I_{C1} \cong (1 + \beta) I_{C1} \\
 V_{CC} &= I_1 R_1 + V_{BE1} + V_i = R_1 (1 + \beta) I_{C1} \\
 &\quad + V_{BE1} + V_i \\
 I_{C1} &= \frac{V_{CC} - V_i - V_{BE1}}{(1 + \beta) R_1} \\
 V_o &= R_2 I_{E2} = R_2 (1 + \beta) I_{B2} \\
 &= R_2 (1 + \beta) I_{C1} \\
 &= \frac{(V_{CC} - V_i - V_{BE1})(1 + \beta) R_2}{(1 + \beta) R_1} \\
 V_o &= \frac{(V_{CC} - V_i - V_{BE1}) R_2}{R_1}
 \end{aligned}$$

12. Draw the output wave shapes of the voltage follower using op-amp with 1 V/ms slew rate with the square wave input shown in **Fig. 15.109(a)**.


*Solution:*

It is seen from the wave shapes of  $v_o$  that remarkable distortion occurs for slew rate at high frequency. **Fig. 15.109(b)** is 100 Hz signal that does not produce appreciable distortion. A 10 kHz signal produces appreciable distortion as shown in **Fig. 15.109(c)**. A 1 MHz signal becomes sawtooth wave as in **Fig. 15.109(c)**.


**Figure 15.109(a). Figure 15.109(a)**

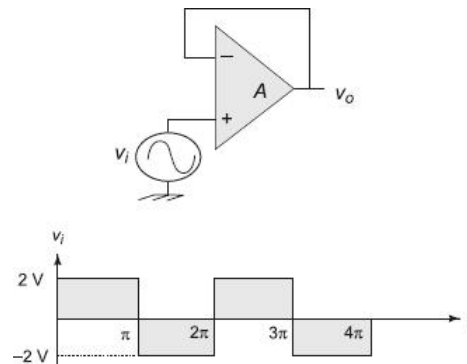

**Figure 15.109(b). Figure 15.109(b)**

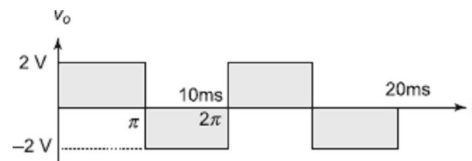

**Figure 15.109(c). Figure 15.109(c)**

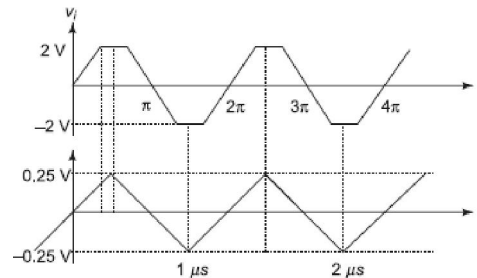


- 13.** A square wave input of 8 V peak to peak magnitude and frequency 2 MHz is applied to a voltage follower which produces the triangular output as shown in **Fig. 15.110**. What is its slew rate?

*Solution:*

$$SR = \frac{4 \text{ V}}{(0.5/2) \mu s} = 16 \text{ V}/\mu s$$

**Figure 15.110. Figure 15.110**

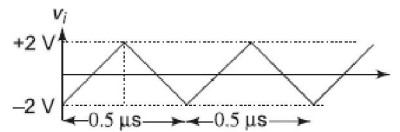

- 14.** The 741 op-amp is used as an inverting amplifier with its gain = 50. What would be the maximum input signal magnitude applied to it if its voltage gain is flat upto 100 kHz?

*Solution:*

Slew rate of the 741 = 0.5 V/μs,

$$SR = 2\pi f V_m = \frac{2\pi f V_{i(pp)}}{10^6},$$

$$V_{i(pp)} = \frac{SR (V/\mu s) \times 10^6}{6.28 \times 100 \times 10^3} = \frac{0.5 \times 10}{6.28}$$

$$= 0.796 \text{ V}$$

The maximum input signal to get undistorted output should be  $\frac{0.796}{50} = 15.9 \text{ mV}$ .

- 15.** A peak to peak input signal of 500 mV has to produce a peak to peak undistorted output voltage of 3 V with a rise time of 4 ms. Can 741 be used for such application?

*Solution:*


$$\text{Rise time} = 3 \text{ V (90\% - 10\%)} = 3 \text{ V (0.90 - 0.10)} = 2.4 \text{ V}$$

$$SR = \frac{2.4}{4 \mu s} = 1.8 \text{ V}/\mu s$$

The 741 cannot be used.

- 16.** The characteristic of the diode is given by the relationship as  $I_D = I_S(e^{qV/\eta kT} - 1)$ , where  $V$  is the forward voltage and  $\eta$  is the ideality factor = 1 (Ge) and 2 (Si). Express  $V_o$  as a function of  $V_i$ . What is the value of input voltage to result in output voltage  $V_o$

$$= 0, \text{ if } R = 100 \text{ K}\Omega, I_S = 1 \text{ }\mu\text{A and } \frac{KT}{q} = 26 \text{ mV.}$$

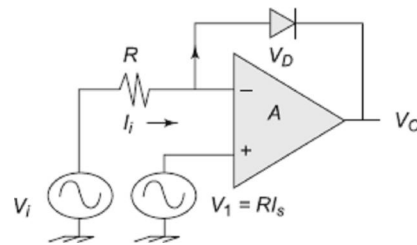**Figure 15.111. Figure 15.111**

$$\begin{aligned} e^{qV/KT} &= \frac{I_D}{I_S} + 1, V = \frac{KT}{q} \ln \left( \frac{I_D}{I_S} + 1 \right) \\ &= 0.026 \ln \left( \frac{I_D}{I_S} + 1 \right) \\ V_D &= 0.026 \left[ \ln \left( \frac{I_D}{I_S} \right) + \ln 1 \right] \\ &= 0.026 \left[ \ln \left( \frac{I_D}{I_S} \right) + 0 \right] \\ V_O = V_D &= 0.026 \ln \left( \frac{I_D}{I_S} \right), I_D = \frac{V_i}{R} = I_i \\ \text{(a) } V_O = V_D &= 0.026 \ln \left( \frac{V_i}{RI_S} \right) = 0 \end{aligned}$$

$$\begin{aligned} &= \ln \left( \frac{V_i}{RI_S} \right) = \ln 1, \\ V_i = RI_S &= 10^5 \times 10^{-6} = 0.1 \text{ V} \end{aligned}$$


17. In the circuit of Fig. 15.112 the output voltage  $V_o$  is initially zero. The switch is connected first to A to charge the capacitor  $C_1$  to the voltage  $V$ . It is then connected to point B. This process repeats  $f$  times per second. Calculate (a) transfer of charge per second from A to B, (b) Derive the average rate of change of the output voltage  $V_o$ , (c) If the switch and capacitor are removed and a resistor is connected between point A and B, what will be the value of resistor to get the same average rate of change the output voltage, (d) If the repetition rate of the switching action is  $10^4$  times per second,  $C_1 = 100 \text{ pF}$ ,  $C_2 = 10 \text{ pF}$  and  $V = 10 \text{ mV}$ , what is the average rate of change of the output voltage?

*Solution:*

(a) When the switch changes from B to A  $f$  times per second, the charge transferred to the capacitor  $C_1 = Qf = C_1 Vf$ . The capacitor charges exponentially, but the time constant of charging is zero and hence capacitor charges instantaneously.

$$\begin{aligned} V &= V_{SS}(1 - e^{-t/RC}) = V_{SS}(1 - e^{-t/0}) \\ &= V_{SS} = \frac{Q}{C_1} \end{aligned}$$

**Figure 15.112. Figure 15.112**

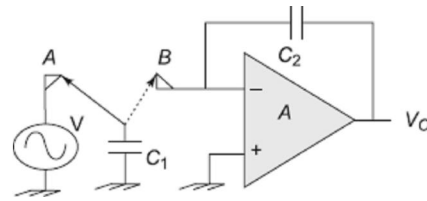

(b)

$$i = -C_2 \frac{dV_o}{dt}, \frac{dV_o}{dt} = -\frac{i}{C_2},$$

$$dV_o = -\frac{idt}{C_2} = -\frac{Q}{C_2} = -\frac{C_1 Vf}{C_2}$$

(c)

$$i = V/R, dV_o = -\frac{idt}{C_2} = -\frac{Vdt}{RC_2}$$

$$= -\frac{V}{RC_2} \text{ in one second}$$

$$\text{Equating } dV_o \text{ yields as } -\frac{V}{RC_2} = -\frac{C_1 Vf}{C_2}, R = \frac{1}{C_1 f}$$

The integration of the steady input voltage gives ramp (rate of change) voltage.


(d)

$$dV_o = -\frac{C_1 Vf}{C_2}$$

$$= -10 \times 10^{-3} \times 10^4 \frac{100}{10} = -1000 \text{ V}$$

**18.** Show that the circuit in **Fig. 15.113** simulates an inductance across its input terminals.

**Figure 15.113. Figure 15.113**

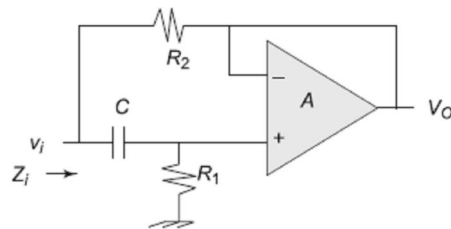


*Solution:*

$$i_i = \frac{v_i - v_o}{R_2} + SC(v_i - v_+), v_+ = v_o$$

$$\begin{aligned}
 & \text{(as unity gain), } v_+ = \frac{SCR_1 v_i}{1 + SCR_1} \\
 i_i &= \left( \frac{1}{R_2} + SC \right) v_i - \left( \frac{1}{R_2} + SC \right) v_+ \\
 &= \frac{1 + SCR_2}{R_2} v_i - \frac{1 + SCR_2}{R_2} v_+ \\
 &= \frac{1 + SCR_2}{R_2} v_i - \left( \frac{1 + SCR_2}{R_2} \right) \frac{SCR_1}{1 + SCR_1} v_i \\
 &= \frac{1 + S^2 C^2 R_1 R_2 + SC(R_1 + R_2)}{-SCR_1 - S^2 C^2 R_1 R_2} v_i \\
 &= \frac{1 + SCR_2}{R_2(1 + SCR_1)} v_i \\
 \text{Hence, } Z_i &= \frac{v_i}{i_i} = \frac{(1 + SCR_1)R_2}{1 + SCR_2}
 \end{aligned}$$

Figure 15.114. Figure 15.114

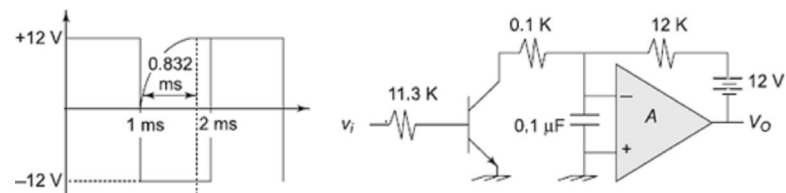

**Solution:**

When input is changing from  $-12\text{ V}$  to  $+12\text{ V}$ , the capacitor gets charged to the maximum voltage exponentially with the time constant  $= 12\text{ K} \times 0.1 \times 10^{-6} = 1.2\text{ ms}$ . In order to find out the time taken by the capacitor to reach final value  $= 12\text{ V}$ , we have to see the following expression  $V_C = V_F - (V_F - V_i)e^{-t/RC}$ ,

$$\begin{aligned}
 &= \frac{(1 + j\omega CR_1)R_2}{1 + j\omega CR_2} \\
 &= \frac{(1 + j\omega CR_1)R_2(1 - j\omega CR_2)}{(1 + j\omega CR_2)(1 - j\omega CR_2)} \\
 &= \frac{(1 + \omega^2 C^2 R_1 R_2 + j\omega C(R_1 - R_2)R_2)}{1 + \omega^2 C^2 R_2^2} \\
 &= R + j\omega L \\
 \text{where, } R &= \frac{(1 + \omega^2 C^2 R_1 R_2)R_2}{1 + \omega^2 C^2 R_2^2}, \\
 \text{and } L &= \frac{C(R_1 - R_2)R_2}{1 + \omega^2 C^2 R_2^2}
 \end{aligned}$$

- 19.** Draw the waveform of  $v_o(t)$  as function of  $v_i$ . Specifying the output voltage  $v_o(t)$ , determine the voltage levels and time constants involved.


$$\begin{aligned}
 e^{-t/RC} &= \frac{V_F - V_C}{V_F - V_i}, \\
 t &= RC \ln \frac{V_F - V_i}{V_F - V_C} = RC \ln \frac{12 - (-12)}{12 - 0} \\
 &= RC \ln 2 \\
 &= 12 \times 10^3 \times 0.1 \times 10^{-6} \times 0.693 \\
 &= 0.832\text{ ms}
 \end{aligned}$$

As the capacitor gets charged from  $-12\text{ V}$  to slightly above  $0\text{ V}$ , the output amplifier gets saturated.

When the capacitor is charged to  $+12\text{ V}$ , the capacitor starts discharging through saturated transistor with a time constant  $= 100 \times 0.1 \times 10^{-6} = 0.01\text{ ms}$

20. Show that circuit of Fig. 15.115 simulates an inductor i.e.  $\frac{v_i(s)}{i_i(s)}$  is inductive.

Figure 15.115. Figure 15.115

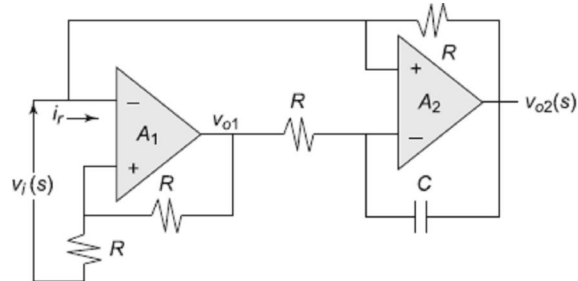

Solution:

$$v_{o1} = v_i \left( 1 + \frac{R}{R} \right) = 2v_i$$

$$v_{o2} = -\frac{1}{CR} \int v_{o1} dt = -\frac{v_{o1}}{SCR} = -\frac{2v_i(s)}{SCR}$$

$$\text{or, } v_{o2} = -i_i R = -\frac{2v_i(s)}{SCR}$$

$$\text{or, } \frac{v_i(s)}{i_i(s)} = SCR^2/2 = j\omega CR^2/2 = j\omega L$$

$$\text{where } L = CR^2/2$$

21. How much is the output voltage in the circuit of Fig. 15.116.

Solution:

Writing node equation at the inverting input terminal of the op-amp results as

$$\frac{v_i - v_-}{5\text{ K}} = \frac{v_- - v_o}{10\text{ K}}, \left( \frac{1}{5\text{ K}} + \frac{1}{10\text{ K}} \right) v_-$$

$$= \frac{v_i}{5\text{ K}} + \frac{v_o}{10\text{ K}}$$

$$\text{or, } v_- = \frac{10v_i}{15} + \frac{5v_o}{15} = v_+ \cong \frac{10}{100} v_o$$


$$\left( \frac{1}{10} - \frac{5}{15} \right) v_o = \left( \frac{15 - 50}{150} \right) v_o$$

$$= \left( \frac{-35}{150} \right) v_o = \frac{10 \times 2}{15}$$

$$v_o = -\frac{10 \times 2}{15} \times \frac{150}{35} = -\frac{10 \times 2 \times 10}{35}$$


$$= -6.5\text{ V}$$

Figure 15.116. Figure 15.116

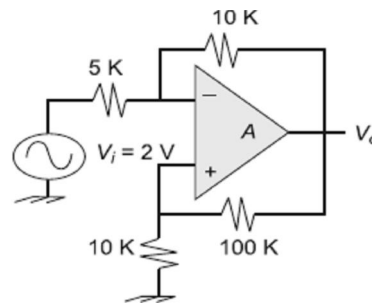

22. Obtain the value of resistor  $R$  for the condition that both inputs  $V_-$  and  $V_+$  should be amplified by the same amount in **Fig. 15.117**.

**Figure 15.117. Figure 15.117**

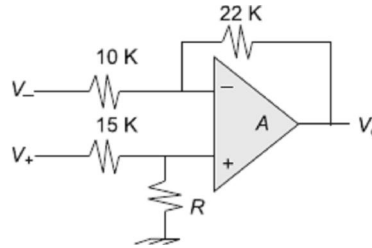

$$\text{For } V_- = 0, V_o = \left(1 + \frac{22}{10}\right) \frac{R}{R+15} V_+$$

$$= \frac{3.2R}{R+15} V_+$$

$$\text{For } V_+ = 0, V_o = -\frac{22}{10} V_- = -2.2 V$$


$$\frac{V_o}{V_+} = \frac{3.2R}{R+15} = \frac{V_o}{V_-} = 2.2,$$

$$3.2R - 2.2R = 33$$

$$\text{or, } R = 33 \text{ K}\Omega$$

23. Derive a relationship between the input and output voltages for the circuit shown in **Fig. 15.118**. Also obtain the output waveform for a symmetrical square wave input voltage of amplitude  $V_p$  and frequency  $f$ .

**Figure 15.118. Figure 15.118**

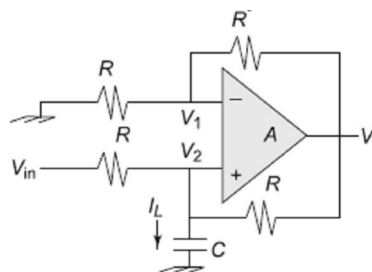

*Solution:*



$$V_1 = \frac{R}{2R} V_o = \frac{V_o}{2}, \frac{V_{in} - V_2}{R} + \frac{V_o - V_2}{R}$$

$$= I_L, V_1 = V_2$$

$$\frac{V_{in}}{R} - \frac{V_o}{2R} - \frac{V_o}{2R} + \frac{V_o}{R} = I_L$$

$$\text{or, } I_L = \frac{V_{in}}{R} = C \frac{dV_2}{dt}, V_2 = \frac{1}{RC} \int V_{in} dt$$

$$V_o = 2V_2 = \frac{2}{RC} \int V_{in} dt$$

If the input voltage is square wave, the output voltage is a triangular wave of magnitude  $\pm V_P$  and frequency  $f$ .

24. Find out the value of two resistors used in a non-inverting op-amp to result in the voltage gain of 21 dB.

*Solution:*


$$21\text{dB} = 10^{21/20} = 10^{1.05} = 11.22$$

$$= 1 + \frac{R_2}{R_1}, R_2 = 10.22 R_1$$

$$\text{If } R_1 \text{ is selected to be } 10 \text{ K}\Omega, R_2 = 102.2 \text{ K}\Omega$$

25. Obtain the transfer function between input and output voltages of Fig. 15.119. What will be the value of the capacitor required to yield a phaseshift of  $270^\circ$  at a frequency of 1 kHz with  $R = 10 \text{ K}$ ?

**Figure 15.119.** Figure 15.119

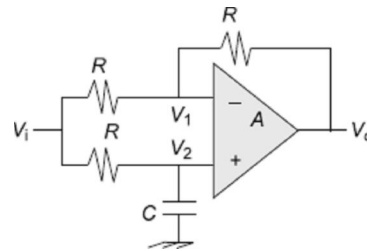

*Solution:*

$$v_2 = \frac{v_i / SC}{R + \frac{1}{SC}} = \frac{v_i}{1 + SCR}$$

$$\frac{v_i - v_1}{R} = \frac{v_1 - v_o}{R},$$

$$2v_1 = v_i + v_o$$

$$\frac{v_i + v_o}{2} = \frac{v_i}{1 + SCR},$$

$$v_o + v_i = \frac{2v_i}{1 + SCR},$$

$$v_o = \frac{2v_i}{1 + SCR} - v_i$$

$$v_o = \frac{(2 - 1 - SCR)v_i}{1 + SCR} = \frac{(1 - SCR)v_i}{1 + SCR}$$

$$\text{or, } \frac{v_o}{v_i} = \frac{1 - SCR}{1 + SCR} = \frac{1 - j\omega CR}{1 + j\omega CR}$$

$$= \frac{\sqrt{1 + (\omega CR)^2}}{\sqrt{1 + (\omega CR)^2}} = 1$$

$$\text{Phase shift} = -\tan^{-1} \omega CR - \tan^{-1} \omega CR$$

$$= -2 \tan^{-1} \omega CR = 270^\circ$$

$$\text{or, } -\tan^{-1} \omega CR = 135^\circ, \tan 135 = -1$$

$$= -\omega CR$$


$$C = \frac{1}{2\pi \times 1000 \times 10K} = \frac{0.159}{10^7}$$

$$= 0.159 \times 10^{-7}$$

$$C = 0.159 \times 10^{-7} = 0.0159 \mu F$$


The plots of magnitude and phase shift are shown in **Fig. 15.120**.

**Figure 15.120. Phase and magnitude plot of given circuit**

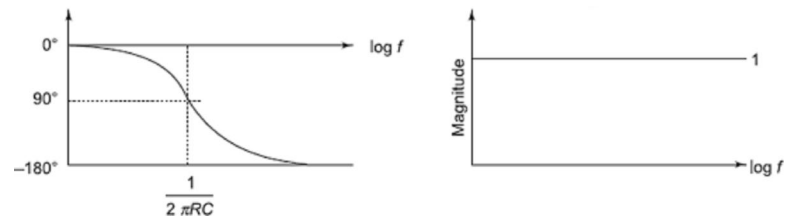

**26.** Obtain the transfer function between input and output voltages of **Fig. 15.121**.

**Figure 15.121. Figure 15.121**

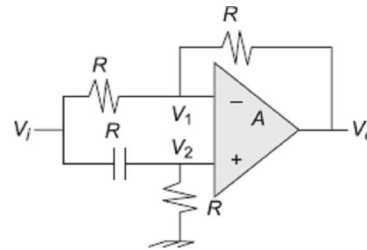

*Solution:*

$$v_2 = \frac{v_i R}{R + \frac{1}{SC}} = \frac{v_i SCR}{1 + SCR}, \frac{v_i - v_1}{R}$$

$$= \frac{v_i - v_o}{R}, 2v_1 = v_i + v_o$$

$$\frac{v_i + v_o}{2} = \frac{v_i SCR}{1 + SCR},$$

$$v_o + v_i = \frac{2v_i SCR}{1 + SCR},$$

$$v_o = \frac{2v_i SCR}{1 + SCR} - v_i$$

$$= \frac{(2SCR - 1 - SCR)v_i}{1 + SCR}$$

$$= \frac{(SCR - 1)v_i}{1 + SCR}$$


$$\text{or, } \frac{v_o}{v_i} = \frac{SCR - 1}{1 + SCR} = \frac{-1 + j\omega CR}{1 + j\omega CR}$$

$$= -\frac{\sqrt{(-1)^2 + (\omega CR)^2}}{\sqrt{1 + (\omega CR)^2}} = -1$$

$$\text{Phase shift} = 180^\circ - \tan^{-1} \omega CR - \tan^{-1} \omega CR = 180^\circ - 2 \tan^{-1} \omega CR$$


The plots of its magnitude and phase-shift are shown in **Fig. 15.122**.

**Figure 15.122. Phase and magnitude plot of given circuit**

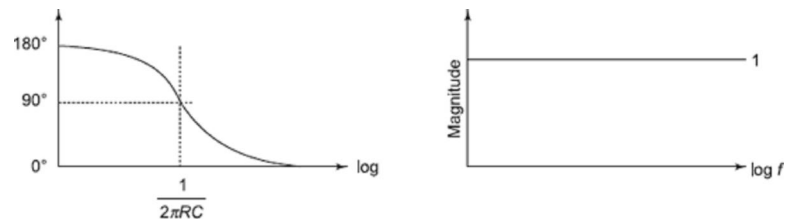

27. What value of the resistance  $R_B$  will provide balance of the bridge yielding  $V_o = 0$  for  $R_A = R_C = R_D = 1 \text{ K}\Omega$ . What will be the value of output voltage, if now  $R_B$  is set to  $0.5 \text{ K}\Omega$ ?

**Figure 15.123. Figure 15.123**

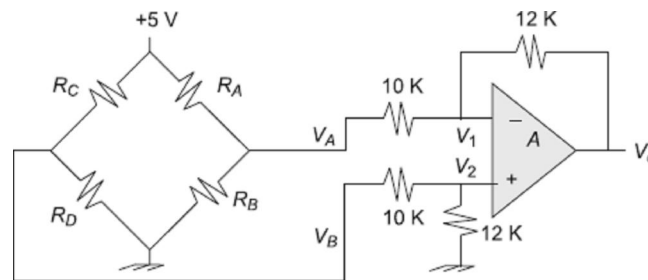

*Solution:*

$$V_B = \frac{5VR_D}{R_C + R_D} = 2.5 \text{ V}$$

$$V_A = \frac{5VR_B}{R_A + R_B} = \frac{5VR_B}{1 \text{ K} + R_B}$$

$$V_2 = \frac{V_B 12}{12 + 10} = \frac{12V_B}{22}$$

$$\frac{V_A}{10} + \frac{V_o}{12} = V_1 \left( \frac{1}{10 \text{ K}} + \frac{1}{12 \text{ K}} \right)$$

$$V_1 = \frac{12V_A}{22} + \frac{10V_o}{22} = \frac{12V_B}{22}, 10V_o$$

$$= 12(V_B - V_A), V_o = 1.2 (V_B - V_A),$$

For the condition  $V_o = 0$

$$= 1.2 \left( 2.5 - \frac{5R_B}{R_A + R_B} \right), R_A + R_B = 2R_B,$$

$$R_A = R_B = 1 \text{ K}\Omega$$

$$V_o = 1.2 \left( 2.5 - \frac{5 \times 0.5}{1.5} \right) = 1.2(2.5 - 1.67) = 0.996 \text{ V}$$

28. Sketch the waveform of the output voltage for the circuit of **Fig. 15.124**. What portion of the current  $i_o$  coming out from the operational amplifier flow as the load current  $i_L$ ?

*Solution:*

$$\text{For } V_{in} = 0, V_o = \frac{-10 \times 12}{120} = -1 \text{ V},$$


$$T = \frac{1}{100} = 10 \text{ ms}$$

$$V_{in} = 12 = 0,$$

$$V_o = \frac{-10 \times 0.1 \cos 2\pi \times 100t}{1}$$

$$= -1(\cos 2\pi \times 100t) \text{ V}$$

**Figure 15.124. Figure 15.124**

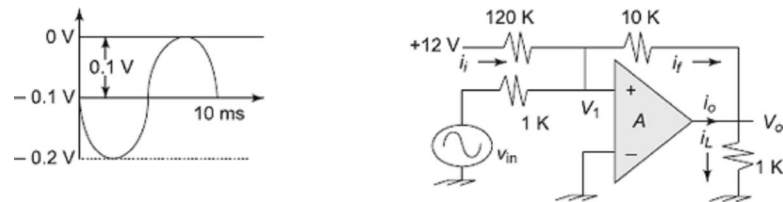

$$i_L = \frac{v_o}{R_L} = i_o + i_f = i_o + \frac{v_o}{R_F},$$

$$i_o = \frac{V_o}{R_L} - \frac{V_o}{R_F} = \frac{V_o}{1 \text{ K}} - \frac{V_o}{10 \text{ K}} \cong \frac{V_o}{R_L}$$

$$i_o = \frac{V_o}{R_L} = \frac{R_F i_f}{R_L}$$

$$= \frac{R_F}{R_L} \times \frac{V_i}{R_i}$$

$$= \frac{10 \text{ K}}{1 \text{ K}} \times \frac{12}{120 \text{ K}} = 1 \text{ mA (max)},$$

$$i_i = \frac{12}{120 \text{ K}} = 0.1 \text{ mA} = i_f,$$


$$i_L = i_o - i_f = 1 \text{ mA} - 0.1 \text{ mA} = 0.9 \text{ mA}$$

Hence,  $i_o = 1 \text{ mA} \cos 2\pi \times 100t$ , now  $i_L = i_o (\text{max}) - i_f = 1 \text{ mA} - 0.1 \text{ mA} = 0.9 \text{ mA}$

Hence, total  $i_L (\text{max}) = 0.9 \text{ mA} + 0.9 \text{ mA} = 1.8 \text{ mA}$ .

29. Determine the output voltage  $v_o$  for the circuit shown in **Fig. 15.125**.

**Figure 15.125. Figure 15.125**

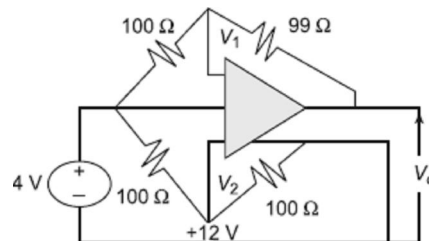

**Solution:**

$$V_2 = \frac{4 \text{ V} \times 100}{200} = 2 \text{ V}, \frac{V_1 - V_1}{100} = \frac{V_1 - V_o}{99}$$


$$V_1 \left( \frac{1}{100} + \frac{1}{99} \right) = \frac{4}{100} + \frac{V_o}{99}$$

$$\text{or, } V_1 = \frac{4 \times 99}{199} + \frac{V_o \times 100}{199} = 2 \text{ V}$$

$$\text{or, } V_o = (2 - 1.99)1.99 = 0.02 \text{ V}$$

30. Show that the system shown in **Fig. 15.126** is a double integrator. In other words, prove that the transfer gain is given by  $\frac{V_o}{V_i} = \frac{-1}{C^2 R^2 S^2}$ , assume an ideal op-amp.

**Figure 15.126. Figure 15.126**

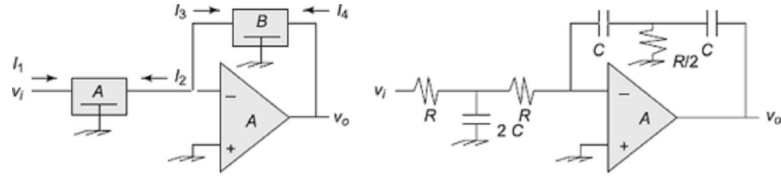

*Solution:*

$$I_2 + I_3 = 0, Y_{21A} = \frac{I_2}{V_i}, I_2 = Y_{21A} V_i,$$

$$\frac{I_3}{V_o} = Y_{12B},$$

$$I_3 = Y_{12B} V_o, V_i Y_{21A} + V_o Y_{12B} = 0$$

$$\text{or, } \frac{V_o}{V_i} = -\frac{Y_{21A}}{Y_{12B}}. \text{ In } T\text{-network, } Z_1$$

and  $Z_2$  are series elements and  $Z_1$  is shunt element.

$$Y_{12} = Y_{21} = -\frac{Z_3}{\Delta Z}$$

$$= -\frac{Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}$$

Now,

$$Y_{21A} = -\frac{1/2SC}{R^2 + \frac{R}{2SC} + \frac{R}{2SC}}$$

$$= -\frac{1/2SC}{R^2 + \frac{2R}{2SC}} = -\frac{1}{2R(SCR + 1)}$$

$$Y_{12B} = -\frac{R/2}{\frac{1}{S^2 C^2} + \frac{R}{2SC} + \frac{R}{2SC}}$$

$$= -\frac{R/2}{\frac{1}{S^2 C^2} + \frac{R}{SC}} = -\frac{R/2}{\frac{1 + SCR}{S^2 C^2}}$$

$$= -\frac{RS^2 C^2}{2(1 + SCR)}$$


$$\text{Hence, } \frac{V_o}{V_i} = -\frac{Y_{21A}}{Y_{12B}}$$

$$= -\frac{2(SCR + 1)}{2R(SCR + 1)RS^2 C^2} = -\frac{1}{R^2 S^2 C^2}$$

31. Obtain the voltage transfer function between output and input voltages of **Fig. 15.127**. When switch is open, the opamp does not draw any current and hence  $I_2 = 0$ .

*Solution:*

**Figure 15.127. Figure 15.127**

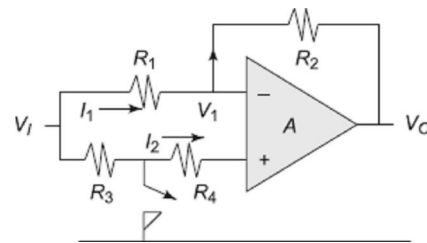

$$\frac{V_i - V_1}{R_1} = \frac{V_1 - V_O}{R_2}, \quad V_1 = \frac{V_i R_2}{R_1 + R_2} + \frac{V_O R_1}{R_1 + R_2}$$

$$V_1 = V_i = \frac{V_i R_1}{R_1 + R_2} + \frac{V_O R_1}{R_1 + R_2}$$

$$\frac{V_i(R_1 + R_2 - R_2)}{R_1 + R_2} = \frac{V_O R_1}{R_1 + R_2}$$

$$\text{or, } \frac{V_O}{V_i} = \frac{R_1}{R_1} = 1.$$


When the switch is closed, the non-inverting input terminal is pulled to ground and hence its gain

$$= -\frac{R_2}{R_1}.$$

- 32.** Obtain voltage gain under the control of voltage applied at the gate of the JFET in **Fig. 15.128**. When control signal = 0, the JFET offers minimum drain resistance and hence non-inverting input terminal is pulled to approximately ground. Thus,  $\frac{V_O}{V_i} = -\frac{R_2}{R_1}$ .

*Solution:*

**Figure 15.128. Figure 15.128**

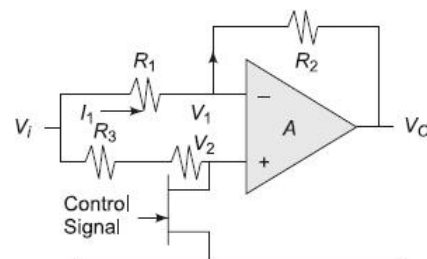

When the control signal is high, it reduces the channel width and provides very large resistance to provide open circuit, thus  $V_1 = V_2 = V_i$ .

$$\text{Hence, } \frac{V_O}{V_i} = \frac{R_1}{R_1} = 1.$$


- 33.** Find the condition of input voltage for making the LED ON in **Fig. 15.129**.

*Solution:*

$$V_1 = \frac{10 \times 10}{20} = 5 \text{ V.}$$

Hence, LED will glow if  $V_i > 5 \text{ V}$ .


**Figure 15.129. Figure 15.129**

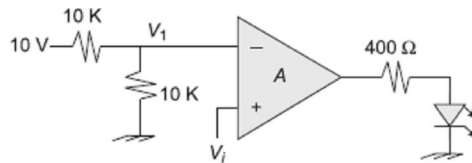

34. What will be the value of input voltage  $V_i$  such that the LED in Fig. 15.130 starts glowing.

LED will glow if  $V_i > 5$  V.

Figure 15.130. Figure 15.130

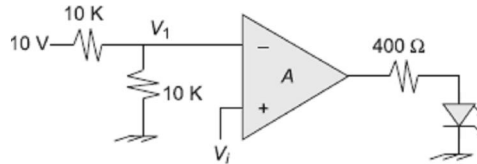


35. An op-amp with a slew rate of 1.5 V/ms has been used as an inverting amplifier with gain of 10. What is the maximum input signal if the frequency of input signal is 1 kHz?

$$\begin{aligned}\omega_{\max} &= \frac{MSR}{V_m}, V_m = \frac{MSR}{\omega_{\max}} \\ &= \frac{1.5}{10^{-6} \times 2\pi \times 1 \text{ K}} = \frac{0.159 \times 1.5}{10^{-3}} \\ &= 0.2385 \times 10^3.\end{aligned}$$

36. Calculate the voltages  $V_1$  and  $V_O$  in Fig. 15.131.


$$\begin{aligned}V_1 &= \frac{2 \times 10}{20} = 1 \text{ V}, V_O = \left(1 + \frac{50}{20}\right) 2 \text{ V} \\ &= 7 \text{ V}\end{aligned}$$

Figure 15.131. Figure 15.131

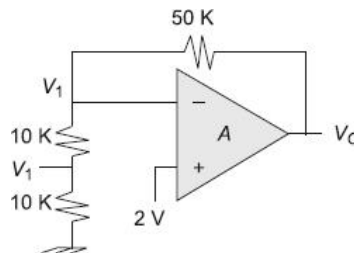

37. When will the output get saturated in Fig. 15.132?

Figure 15.132. Figure 15.132

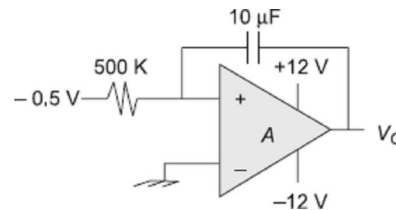


$$\begin{aligned}V_o &= -\frac{1}{RC} \int (-0.5) dt = 12 = \frac{0.5}{5} \int dt, \\ t &= 120 \text{ s}.\end{aligned}$$

38. The switch was closed initially for 0.5 minutes and then opened. What will be the input

voltage if the output in **Fig. 15.133** is initially 0 and  $-5.4$  V after the switch is opened.

$$\begin{aligned} V_o &= -\frac{1}{RC} \int V_i dt = -\frac{V_i}{RC} t = -5.4 \\ &= -\frac{V_i}{500 \times 10^3 \times 30 \times 10^{-6}} 30 \\ &= -\frac{V_i}{5 \times 3} 30 = -2V_i \\ \text{or, } V_i &= \frac{5.4}{2} = 2.7 \text{ V} \end{aligned}$$

**Figure 15.133. Figure 15.133**

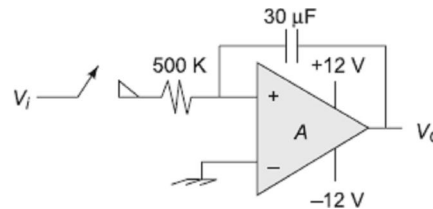


39. A differential amplifier converted to difference amplifier has feedback and input resistor of equal values as in **Fig. 15.134**. What will be the output, if inputs to inverting and non-inverting terminals are  $1.5 \sin \omega t$  and  $1.5 \cos \omega t$ .

*Solution:*

$$\begin{aligned} V_o &= V_2 - V_1 = 1.5 \cos \omega t - 1.5 \sin \omega t \\ &= 1.5(\cos \omega t - \sin \omega t) \\ &= 1.5 \times \sqrt{2} \left( \frac{1}{\sqrt{2}} \cos \omega t - \frac{1}{\sqrt{2}} \sin \omega t \right) \\ &= 1.5 \times \sqrt{2} \left( \cos \frac{\pi}{4} \cos \omega t - \sin \frac{\pi}{4} \sin \omega t \right) \\ &= 2.12 \cos \left( \omega t + \frac{\pi}{4} \right) \end{aligned}$$


**Figure 15.134. Figure 15.134**

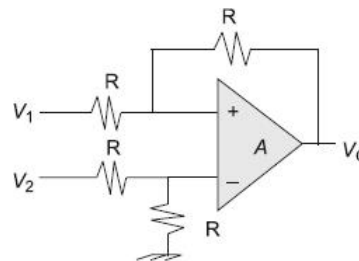

40. The integrator shown in **Fig. 15.135** produces an output voltage  $= V_o = V_m \sin(100t + \phi)$  in response to an input voltage of  $V_i = 0.1 \sin(100t)$ . What is the maximum value of the output voltage?





$$\begin{aligned}
 A_{vCL} &= -\frac{R_2 / (SCR_2 + 1)}{5K} \\
 &= -\frac{50K}{5K(SCR_2 + 1)} = -\frac{10}{(SCR_2 + 1)} \\
 &= -\frac{10}{(j100 \times 0.1 \times 10^{-6} \times 50 \times 10^3 + 1)} \\
 &= -\frac{10}{(j0.5 + 1)} \\
 &= -\frac{10}{(\sqrt{0.5^2 + 1})} = -\frac{10}{(\sqrt{0.25 + 1})} = -8.94 \\
 V_O &= -8.94 \times 0.1 = -0.894 \text{ V} = V_m \\
 &\cong -0.9 \text{ V}
 \end{aligned}$$

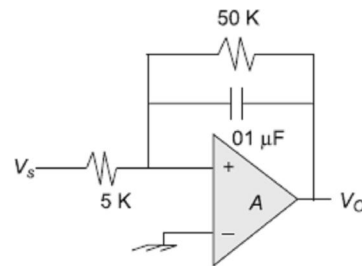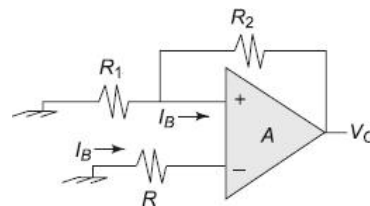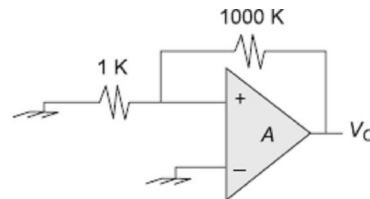**Figure 15.135. Figure 15.135**

41. What is the relationship between resistors  $R$  and  $R_1$  and  $R_2$  in **Fig. 15.136**.

*Solution:*

$$R = R_1 \parallel R_2.$$

**Figure 15.136. Figure 15.136****Figure 15.137. Figure 15.137**

42. The offset voltage to the circuit of **Fig. 15.137** is 1 mV. How much output voltage will be displayed?

*Solution:*

$$\pm \frac{1000}{1} \times 1 \text{ mV} = \pm 1 \text{ V}.$$


43. What would be the frequency of oscillation in **Fig. 15.138**, if  $C = \frac{1}{2\pi} \mu\text{F}$  and  $R = 1 \text{ K}$ ? What would be the minimum gain of the amplifier to sustain oscillations?

$$f = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 10^3 \times \frac{1}{2\pi} \times 10^{-6}}$$


$$= 10^3 \text{ Hz}$$

$$\text{The minimum gain} = 1 + \frac{R_2}{R_1} = 1 + \frac{2R_1}{R_1}$$

$$= 3 \quad (R_2 = 2R_1)$$

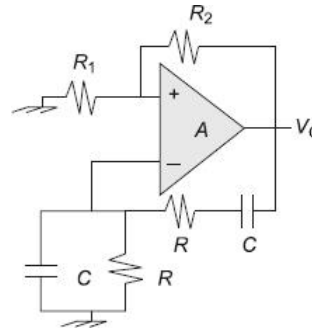**Figure 15.138. Figure 15.138**

44. Calculate the ratio of ON duration to OFF duration of the output waveform of circuit in **Fig. 15.139**.

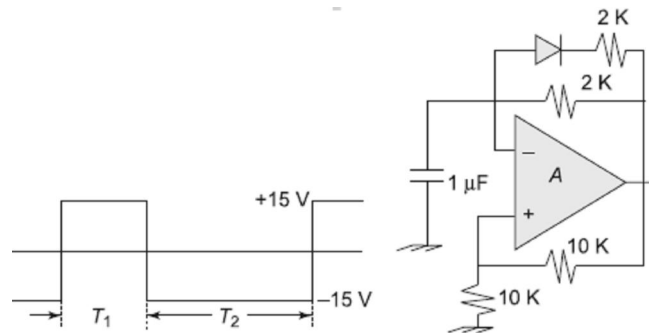**Figure 15.139. Figure 15.139**

$$T_1 = RC \ln \frac{1+\beta}{1-\beta},$$

$$T_2 = RC \ln \frac{1+\beta}{1-\beta},$$

$$\beta = \frac{10 \text{ K}}{10 \text{ K} + 10 \text{ K}} = \frac{1}{2}, RC = 1 \text{ K} \times 1 \mu\text{F}$$

$$= 1 \text{ ms},$$

$$\ln \frac{1+\beta}{1-\beta} = \ln 3 = 1.1$$

For  $T_2$  at  $-15 \text{ V}$ , diode is forward biased.  
 $R = 2 \text{ K} \parallel 2 \text{ K} = 1 \text{ K}$

$$\text{Hence, } T_2 = RC \ln \frac{1+\beta}{1-\beta} = 1 \text{ ms} \times 1.1$$

$$= 1.1 \text{ ms},$$

For  $T_1$  at  $+15 \text{ V}$ , diode is off,  $R = 2 \text{ K}$ ,  $RC$   
 $= 2 \text{ K} \times 1 \mu\text{F} = 2 \text{ ms}$

$$T_1 = RC \ln \frac{1+\beta}{1-\beta} = 2 \text{ ms} \times 1.1 = 2.2 \text{ ms},$$

$$\text{Hence, } \frac{T_1}{T_2} = \frac{2.2 \text{ ms}}{1.1 \text{ ms}} = 2$$

45. Obtain CMRR for the circuit shown in **Fig. 15.140**.

$$V_+ = \frac{R_3 V_2}{R_3 + R_2} = V_-$$

$$= \frac{V_1 R_F}{R_1 + R_F} + \frac{V_O R_1}{R_1 + R_F}$$

$$\text{For } V_1 = 0, V_{o2} = \left(1 + \frac{R_F}{R_1}\right) V_+$$

$$= \left(1 + \frac{R_F}{R_1}\right) \frac{R_3}{R_2 + R_3} V_2$$


$$\text{For } V_2 = 0, V_{o1} = -\frac{R_F}{R_1} V_1$$

$$V_o = V_{o1} + V_{o2}$$

$$= -\frac{R_F}{R_1} V_1 + \left(1 + \frac{R_F}{R_1}\right) \frac{R_3}{R_2 + R_3} V_2$$

$$V_2 = V_C + \frac{V_d}{2} \text{ and } V_1 = V_C - \frac{V_d}{2}$$

**Figure 15.140. Figure 15.140**

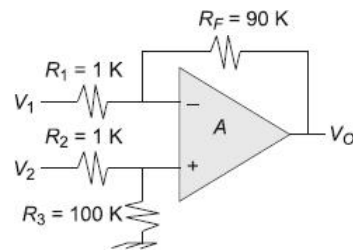


$$V_o = V_{o1} + V_{o2}$$

$$\begin{aligned}
&= -\frac{R_F}{R_1} \left( V_C - \frac{V_d}{2} \right) + \left( 1 + \frac{R_F}{R_1} \right) \frac{R_3}{R_2 + R_3} \left( V_C + \frac{V_d}{2} \right) \\
&= \left[ -\frac{R_F}{R_1} + \left( \frac{R_1 + R_F}{R_1} \right) \left( \frac{R_3}{R_2 + R_3} \right) \right] V_C \\
&\quad + \left[ \frac{R_F}{R_1} + \left( \frac{R_1 + R_F}{R_1} \right) \left( \frac{R_3}{R_2 + R_3} \right) \right] \frac{V_d}{2} \\
&= \frac{(R_1 + R_F)R_3 - R_F(R_2 + R_3)}{R_1(R_2 + R_3)} V_C \\
&\quad + \frac{(R_1 + R_F)R_3 + R_F(R_2 + R_3)}{R_1(R_2 + R_3)} \frac{V_d}{2} \\
A_{DM} &= \frac{V_o}{V_d} \bigg|_{V_C=0} = \frac{V_O}{V_d} \\
&= \frac{(R_1 + R_F)R_3 + R_F(R_2 + R_3)}{2R_1(R_2 + R_3)} \\
A_{CM} &= \frac{V_O}{V_C} \bigg|_{V_d=0} = \frac{V_O}{V_C} \\
&= \frac{(R_1 + R_F)R_3 - R_F(R_2 + R_3)}{R_1(R_2 + R_3)} \\
\text{Hence, CMRR} &= \frac{A_{DM}}{A_{CM}} \\
&= \frac{(R_1 + R_F)R_3 + R_F(R_2 + R_3)}{2\{(R_1 + R_F)R_3 - R_F(R_2 + R_3)\}} \\
&= \frac{(91)100 + 90(101)}{2\{(91 \times 100 - 90(101))\}} \\
&= \frac{(9100 + 9090)}{2(9100 - 9090)} = \frac{18190}{10 \times 2} = 909.5
\end{aligned}$$

46. Obtain the output voltage of the amplifier shown in **Fig. 15.141**


$$\begin{aligned}
v_{o1} &= -\frac{1}{RC} \int v_s dt = -\int v_s dt \\
v_{o1} &= 2 \int v_s dt - 2v_2 - 2v_3
\end{aligned}$$

**Figure 15.141. Figure 15.141**

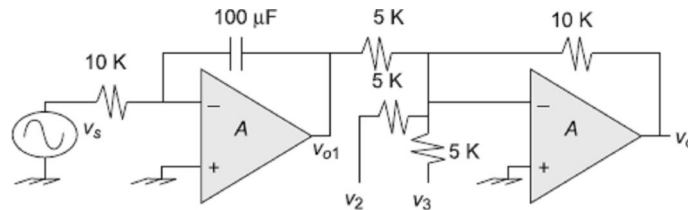

47. The output voltage of Schmitt trigger drawn in **Fig. 15.142** is limited to 10 V and -5 V connecting suitably chosen Zener diodes across the output. What are the upper trip and lower trip voltages of the circuit?

**Figure 15.142. Figure 15.142**

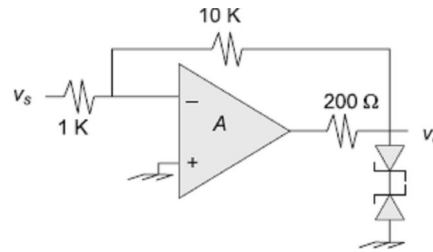

$$V_{UT} = -(-V_{SAT}) \frac{R}{dR}$$

$$= -(-5) \frac{1}{10} = 0.5 \text{ V}$$

$$V_{LT} = -V_{SAT} \frac{R}{dR} = -10 \frac{1}{10} = -1 \text{ V}$$


48. Obtain the output voltage for input voltage  $v_i = \sin \omega t$  applied to the circuit in **Fig. 15.143**.

*Solution:*

For  $v_i > 0$  V, diode is reverse biased, no loop closes.  $v_o = v_i$

For  $v_i < 0$  V, diode is forward biased, loop closes.  $v_o = -v_i$

**Figure 15.143. Figure 15.143**

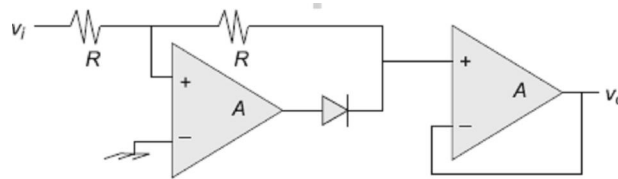


49. Obtain the output voltage of **Fig. 15.144**. What is the name of this circuit?

*Solution:*

For  $V_i > 0$ ,  $D_1$  is forward biased and  $D_2$  is reverse biased,  $V_o = 0$ .

For  $V_i < 0$ ,  $D_1$  is reverse biased and  $D_2$  is forward biased,  $V_o = -\frac{R_2}{R_1} V_i$ . The circuit is a half wave rectifier and conducts for negative half cycle only.


**Figure 15.144. Figure 15.144**

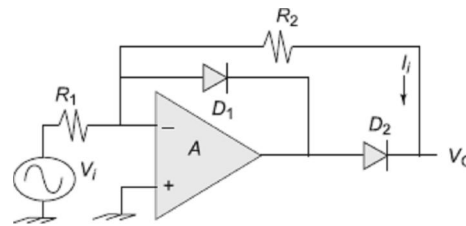

50. What is the ratio of current  $\frac{I_o}{I_i}$  in **Fig. 15.145**.

$$I_o = I_i \frac{R_L}{R_L + R}$$


**Figure 15.145. Figure 15.145**

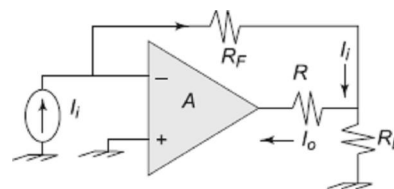

51. Obtain the value of  $R_A$  such that  $V_O = \frac{V_2}{3} - 2V_1$  in Fig. 15.146.

$$\begin{aligned}
 V_+ &= \frac{10KV_2}{10K + R_A} = V_- = \frac{V_1 \cdot 10}{15} + \frac{V_O \cdot 5}{15} \\
 &= \frac{2V_1}{3} + \frac{V_O}{3} \\
 \text{or, } \frac{30V_2}{10 + R_A} &= 2V_1 + V_O, \\
 V_O &= \frac{30V_2}{10 + R_A} - 2V_1 \\
 V_O &= \frac{V_2}{3} - 2V_1 = \frac{30V_2}{10 + R_A} - 2V_1 \\
 \text{or, } \frac{1}{3} &= \frac{30}{10 + R_A}, R_A = 90 - 10 = 80 \text{ K}\Omega
 \end{aligned}$$


Figure 15.146. Figure 15.146

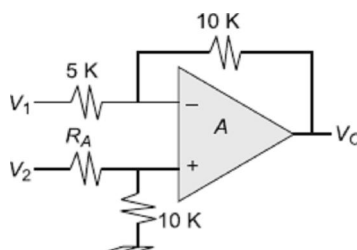

52. What is the value of the output voltage in Fig. 15.147.


$$\begin{aligned}
 \frac{V_1}{2} + \frac{V_1 - V_{01}}{2} + \frac{V_1 - V_2}{1} &= 0 \\
 2V_1 &= \frac{V_{01}}{2} + \frac{V_2}{1} = 0.5 V_{01} + V_2 \\
 V_1 &= 0.25 V_{01} + 0.5 \times 2 \text{ V} = 1 \text{ V} \\
 \text{or, } V_{01} &= 0 \\
 \text{At node 2, } \left( \frac{1}{1} + \frac{1}{2} + \frac{1}{2} \right) V_2 & \\
 &= \frac{V_0}{2} + \frac{V_1}{1} + \frac{V_1}{2} \\
 \text{or, } 2V_2 &= 0.5V_0 + 1 \\
 \text{or, } V_O &= \frac{4-1}{0.5} = 6 \text{ V}
 \end{aligned}$$

Figure 15.147. Figure 15.147

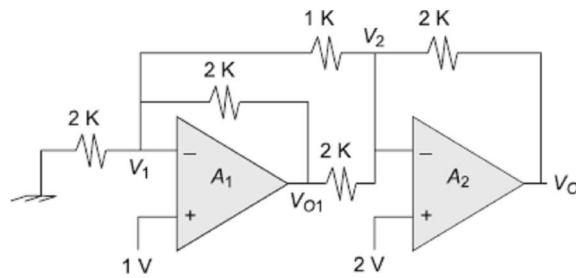

53. Show that  $i_i = D \frac{d^2 v_{in}}{dt^2}$  in Fig. 15.148 assuming all op-amps are ideal. Also show that  $D$  represents a frequency dependent negative resistance.

Figure 15.148. Riordan circuit

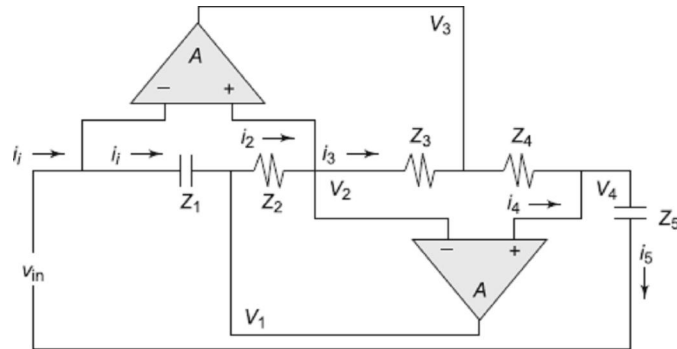

The circuit of Fig. 15.148 can now be analyzed for its input impedance as

$$\begin{aligned}
 v_i &= v_2 = v_4 \\
 (v_i - v_1) &= Z_1 i_1 = Z_1 i_i \\
 (v_2 - v_1) &= -Z_2 i_2 = -Z_2 i_3 = (v_i - v_1) \\
 &= Z_1 i_i, \quad i_3 = -\frac{Z_1}{Z_2} i_i \\
 (v_2 - v_3) &= Z_3 i_3 = (v_4 - v_3) = -Z_4 i_4, \\
 i_4 &= -\frac{Z_3}{Z_4} i_3 \\
 v_4 &= v_i = Z_5 i_5 = Z_5 i_4 \\
 &= Z_5 \frac{Z_3}{Z_4} \times \frac{Z_1}{Z_2} i_i, \\
 i_i &= \frac{Z_2 Z_4}{Z_1 Z_3 Z_5} v_{in} \\
 \text{If } Z_1 &= \frac{1}{SC_1}, \\
 Z_2 &= R = Z_4 = Z_3, \text{ and } Z_5 \\
 &= \frac{1}{SC_2} \text{ are substituted in above, then}
 \end{aligned}$$


$$\begin{aligned}
 i_i &= \frac{S^2 C_1 C_2 R_2 R_4}{R_3} v_{in} \\
 &= D \frac{d^2 v_{in}}{dt^2}, \\
 D &= \frac{C_1 C_2 R_2 R_4}{R_3}, \\
 \frac{i_i}{v_{in}} &= \frac{S^2 C_1 C_2 R_2 R_4}{R_3} \\
 &= \frac{-\omega^2 C_1 C_2 R_2 R_4}{R_3}
 \end{aligned}$$

= negative conductance.

54. Find out the output voltage  $v_o$  for the circuit in Fig. 15.149.

$$\begin{aligned} V_+ &= \frac{V_2}{2}, V_- = V_1 \frac{3}{4} + V_o \frac{1}{4} \\ &= 0.75V_1 + 0.25V_o \\ V_o &= \frac{0.5}{0.25}V_2 - \frac{0.75}{0.25}V_1 \\ &= 2V_2 - 3V_1 \end{aligned}$$

Figure 15.149. Figure 15.149

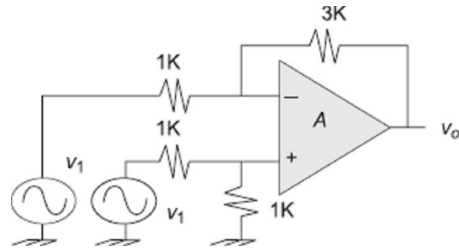


55. Obtain the output voltage of an op-amp summer shown in Fig. 15.150.


$$A_v = 1 + \frac{2R}{R} = 3$$

$$V_o = \left(1 + \frac{2R}{R}\right)(-2 + 2 + \sin \omega t) = 3 \sin \omega t$$


Figure 15.150. Figure 15.150

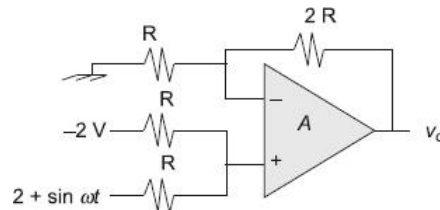

56. Circuit of summing integrator

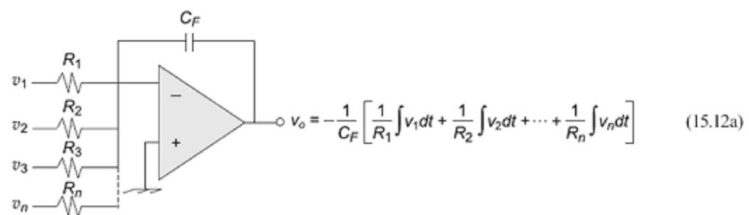

57. Circuit of summing differentiator

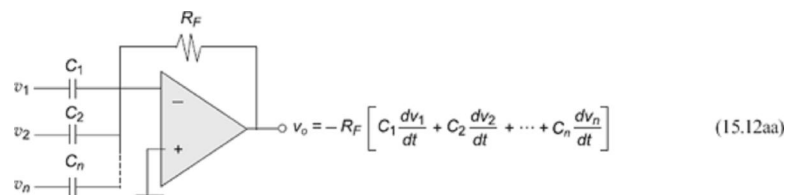



You are currently reading a **PREVIEW** of this book.

Get instant access to over  
\$1 million worth of books and videos.

Start a Free Trial

